

Producing More Electricity with Solar Cells and Solar Panels Answer Sheet Student Activity - Exploration Part 2

10. Voltage for one solar cell _____

11. Current for one solar cell _____

12. Voltage for two solar cells in series _____

13. Current for two solar cells in series _____

14. Voltage for two solar cells in parallel _____

15. Current for two solar cells in parallel _____

16. ___Yes / No , Explain

17.

18.