Producing More Electricity with Solar Cells and Solar Panels Answer Sheet Student Activity - Explanation, Extension, Evaluation

Explanation
1
2
Extension (Draw a diagram or explain connections.)
Evaluation

1. Draw a diagram. Determine number of volts and amps produced.

2. Draw a diagram.	Determine number of volts and amps	s produced.
3. Draw a diagram.	Determine number of volts and amps	s produced.
3. Draw a diagram.	Determine number of volts and amps	s produced.
3. Draw a diagram.	Determine number of volts and amps	s produced.
3. Draw a diagram.	Determine number of volts and amps	s produced.
3. Draw a diagram.	Determine number of volts and amps	s produced.