

Producing More Electricity with Solar Cells and Solar Panels Answer Sheet Student Activity - Exploration Part 1

1. Voltage for one AA battery _____
 2. Current for one AA battery _____
 3. Voltage for two AA batteries in series _____
 4. Current for two AA batteries in series _____
 5. Voltage for two AA batteries in parallel _____
 6. Current for two AA batteries in parallel _____
 7. ___Yes / No , Explain _____
-

8.

9.