

Figure 1. One Battery Voltage Measurement.

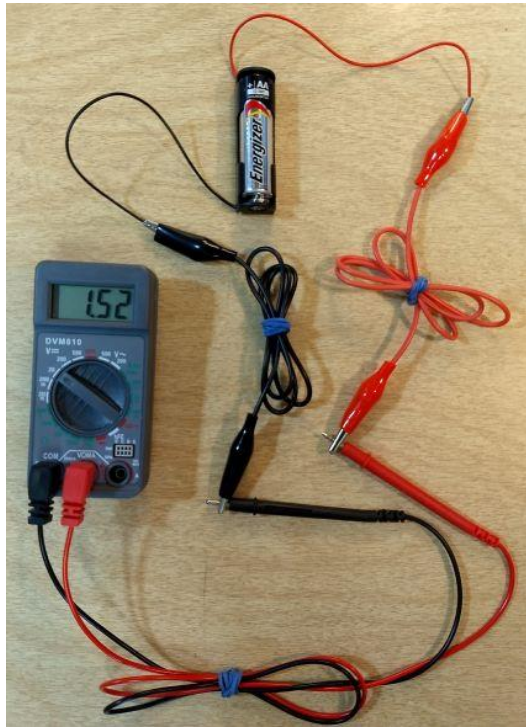


Figure 2. One Battery Current Measurement.

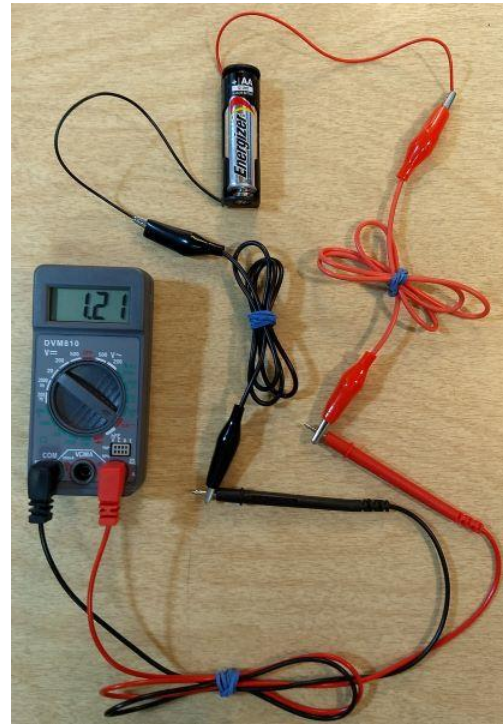


Figure 3. Batteries Connected in Series.

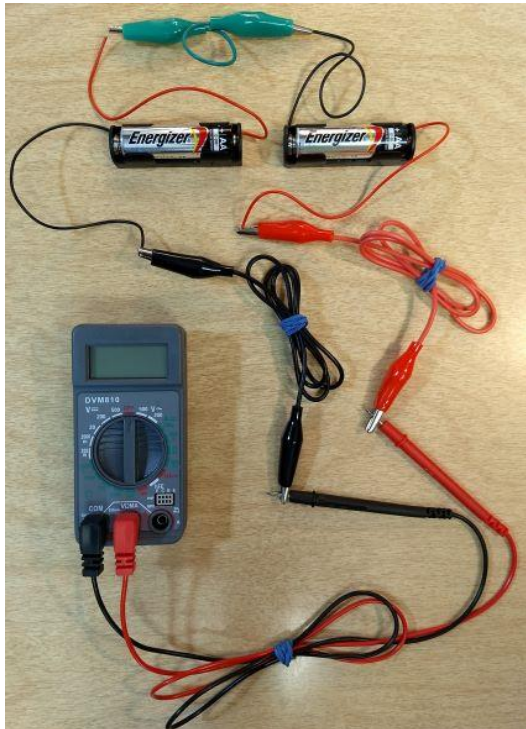


Figure 4. Batteries Connected in Parallel.

